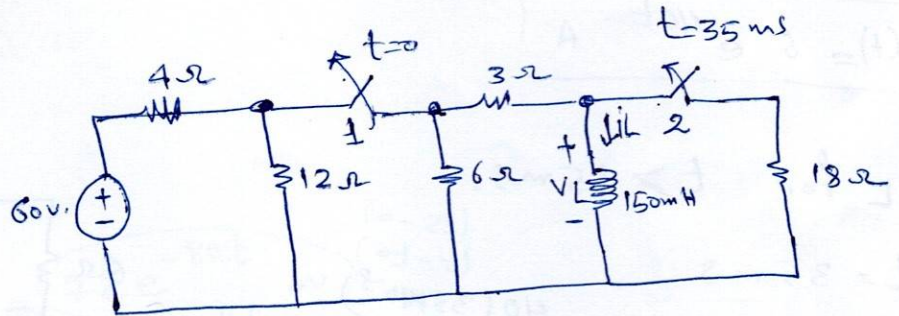


Sequential Switching

Ex: The two switches in the ckt. have been closed along time. At $t=0$, switch 1 is opened. Then, 35 ms later, switch 2 is opened.

- Find $i_L(t)$ for $0 \leq t \leq 35$ ms.
- Find i_L for $t \geq 35$ ms.
- what percentage of the initial energy stored in the 150 mH L is dissipated in the 18 Ω R?




Sol

$t=0 \rightarrow S_1$ opened, after 35 ms $\rightarrow S_2$ is opened
 that's mean at $t < 0$, all the switches were closed for along time
 $S_1, S_2 \rightarrow$ close
 $S_0 \rightarrow$ at $t < 0$
 $I_0 \rightarrow$ we can convert the voltage source to current source.

$$I_S = \frac{V_S}{R} = \frac{60}{4} = 15 \text{ A}$$

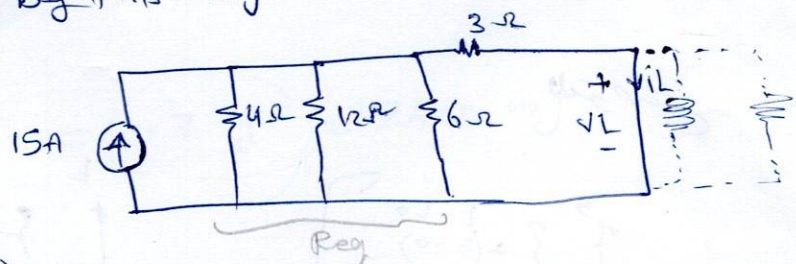$\therefore$ the ckt will become by this fig



$$\therefore I_0 = I_{3\Omega}$$

$$R_{eq} = 6 \parallel 12 \parallel 4 = 2 \Omega$$

$$I_0 = I_{3\Omega} = 15 \times \frac{2}{3+2}$$

$$I_0 = I_S \times \frac{R_{eq}}{R_{eq} + 3}$$

$$I_0 = 6 \text{ A}$$

a) $i_L(t)$ for $0 \leq t \leq 35 \text{ ms}$

$S_1 \rightarrow \text{open}$


$S_2 \rightarrow \text{close}$

$$R_T = (3+6) \parallel 18 = 6 \Omega$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{6} = 25 \text{ ms}, \quad \frac{1}{\tau} = 40 \text{ s}^{-1}$$

$$i_L(t) = I_0 e^{-t/\tau}$$

$$i_L(t) = 6 e^{-40t} \text{ A}$$

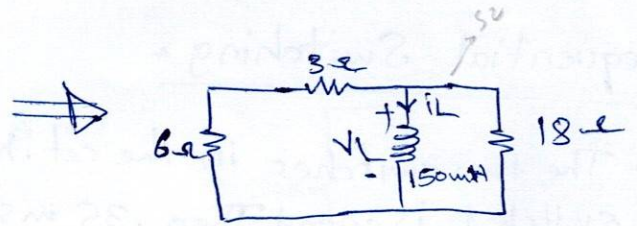


b) i_L for $t \geq 35 \text{ ms}$.

$$t = 35 \text{ ms}$$

$$i_L(35 \text{ ms}) = 6 e^{-40(35 \times 10^{-3})} = 6 e^{-1.4}$$

$$= 1.48 \text{ A} \quad \text{initial } \rightarrow \text{field } t(35-t)$$

$$t \geq 35 \times 10^{-3}$$

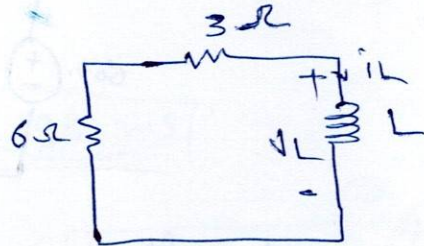



$$R_T = 3+6 = 9 \Omega$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{9} = 16.67 \text{ ms} \Rightarrow \frac{1}{\tau} = 60 \text{ s}^{-1}$$

$$i_L(t) = 1.48 e^{-60(t-0.035)} \text{ A}, \quad t \geq 35 \text{ ms}$$

$$\Rightarrow i(t) = I_0 e^{-(t-t_0)/\tau}$$

توضيح

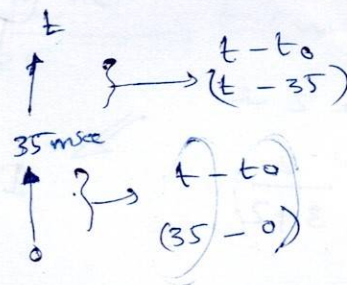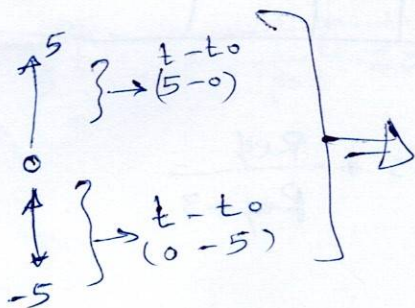

توضيح
للقيمة الموجبة

~~Q.18.2~~ (c) $\frac{w_{18\Omega}}{w_0(L)}$

The R of 18Ω is act only during the interval $0 < t < 35 \text{ ms}$

So, The current was $i_L(t) = 6e^{-40t} \text{ A}$

$$V_L = L \frac{di_L(t)}{dt} \Rightarrow V_L = (150 \times 10^{-3}) \frac{d(6e^{-40t})}{dt}$$

$$V_L = (150 \cdot 10^{-3}) (-240 e^{-40t})$$

$$V_L = -36 e^{-40t} \text{ V}$$

$$P_{18\Omega} = \frac{V_L^2}{18\Omega} = \frac{V^2}{R}$$

$$= \frac{(-36 e^{-40t})^2}{18} = 72 e^{-80t} \text{ W}$$

$$W_{18\Omega} = \int_0^{0.035} P dt$$

$$= \int_0^{0.035} (72 e^{-80t}) dt = -\frac{72}{80} e^{-80t} \Big|_0^{0.035}$$

$$= 0.9(1 - e^{-2.8})$$

$$W_{18\Omega} = 845.27 \text{ mJ}$$

$$w_0 = \frac{1}{2} L I_0^2$$

$$= \frac{1}{2} \cdot (150 \cdot 10^{-3}) \cdot (6)^2 = 2.7 \text{ J} = 2700 \text{ mJ}$$


$$\therefore \frac{w_{18\Omega}}{w_0(L)} = \frac{845.27 \times 10^{-3}}{2.7} \times 100\% = 31.31\%$$

d) Repeat (c) for the 3Ω resistor,

For $0 < t < 35 \text{ msec}$, the voltage across the 3Ω resistor is

$$V_{3\Omega} = V_L \times \frac{3}{3+6}$$
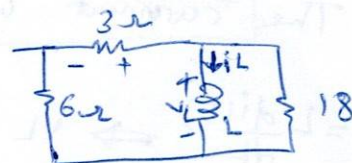
$$= 36e^{-40t} \times \frac{1}{3} = -12e^{-40t} \text{ V.}$$



$$P_{3\Omega} = \frac{V^2}{R} = \frac{(-12e^{-40t})^2}{3} = \frac{144e^{-80t}}{3} \text{ W}$$


$$W_{3\Omega} = \int_0^{0.035} \left(\frac{144e^{-80t}}{3} \right) dt$$

$$= \frac{-144}{3 \times 80} \left[e^{-80t} \right]_0^{0.035}$$

$$= 0.6(1 - e^{-2.8}) = 563.51 \text{ mJ}$$

For $t > 35 \text{ ms}$.
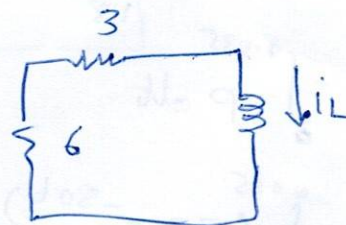
$$i_L = i_{3\Omega} = (1.48e^{-60(t-0.035)}) \text{ A}$$



$$P_{3\Omega} = i^2 \times R$$

$$= (1.48e^{-60(t-0.035)})^2 \times 3$$

$$W_{3\Omega} = \int_{0.035}^{\infty} (1.48e^{-60(t-0.035)})^2 \times 3 dt$$

$$W_{3\Omega} = 54.73 \text{ mJ}$$

* The total energy dissipated in the 3Ω resistor is

$$W_{3\Omega} (\text{total}) = 563.51 + 54.73 = 618.24 \text{ mJ}$$

$$\therefore \frac{W_{3\Omega}}{W_L} \% = \frac{618.24}{2700} \times 100 \% = 22.90 \%$$

e) Repeat for 6Ω

هذه المقاومة هي مرتبطة بالتوالي مع 3Ω. إذن الطاقة المخزنة هي ضعف الموجودة في 3Ω

$$W_{6\Omega} (\text{total}) = 2 \times 618.24 = 1236.48 \text{ mJ}$$

$$1236.48 + 618.24 + 845.27 = 2699.99 \text{ mJ} \approx 2700 \text{ mJ}$$


$$\text{and } \frac{31.31}{18\Omega} + \frac{22.90}{3\Omega} + \frac{45.80}{6} = 100.01 \%$$

والنسبة فيها ضعف
للتحقق من صحة الحساب =

The uncharged capacitor in the ckt. is initially switched to the terminal (a) of the 3 position switch.

Ex: At $t=0$, the switch is moved to position b, where it remains for 15 ms. after the 15 ms delay, the switch is moved to c, where it remains indefinitely.

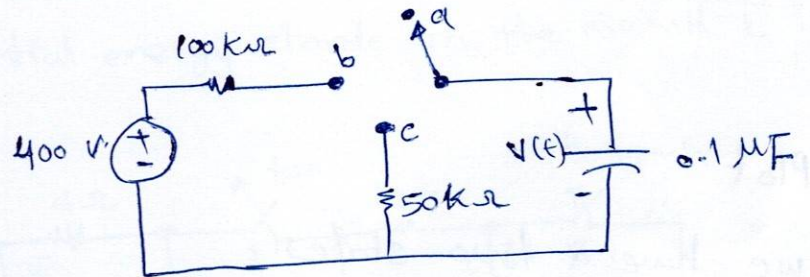a) Derive $V_c(t)$ b) Plot $V_c \propto t$ @ t at $V_c = 200$ V.




Sol: -

→ at $t < 0$

$V_c(0) = 0$ لأن السعة غير مشحونة
بالبداية (الدايرة غير مملوءة)

→ at $t \geq 0$
(0 → 15 ms)

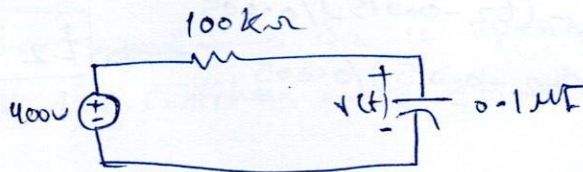

(step)

at $0 \leq t \leq 15$ ms

$$V_c = V_s = 400 \text{ V}$$

$$\tau = RC = 100 \cdot 10^3 \times 0.1 \cdot 10^{-6} = 10 \text{ ms} \quad , \quad \frac{1}{\tau} = 100 \text{ s}^{-1}$$

Step 1


$$V_0 = 0$$

$$V_f = 400$$

$$x(t) = x_f + (x_0 - x_f)e^{-t/\tau}$$

$$V(t) = V_f + (V_0 - V_f)e^{-t/\tau}$$

$$V(t) = 400 + (0 - 400)e^{-100t}$$

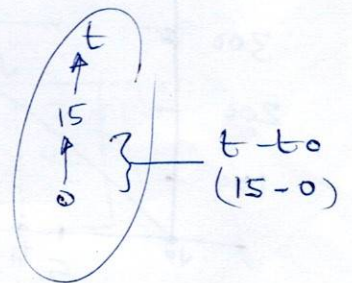

at $0 \leq t \leq 15$

$$V(t) = 400 - 400e^{-100(t-t_0)}$$

$$= 400 - 400e^{-100(15 \cdot 10^{-3} - 0)} \Rightarrow 400 - 400(0.223)$$

$$= 400 - 400 \cdot 0.223$$

$$V(t) = 310.75 \text{ V}$$


at t in position $\underline{c}$

$$t \geq 15$$

$$\tau = RC = 50 \times 10^3 \times 0.1 \times 10^{-6} = 5 \text{ ms}$$

$$V(t) = V_0 e^{-t/\tau}$$
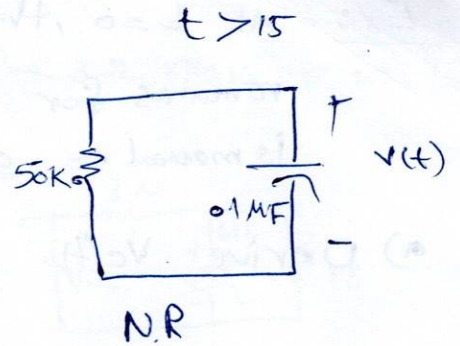
$$V(t) = 310.75 e^{-(t-0.015)/0.005} \text{ V. } t \geq 15 \text{ ms}$$



b) Plot

c) we have a two states

$$V(t) = 400 - 400 e^{-100t}$$

$$200 = 400 - 400 e^{-100t_1} \Rightarrow t_1 = 6.93 \text{ ms}$$

$$V(t) = 310.75 e^{-(t_2-0.015)/0.005}$$

$$200 = 310.75 e^{-(t_2-0.015)/0.005} \Rightarrow t_2 = 17.20 \text{ ms}$$

$$\begin{matrix} \uparrow \\ t \\ 15 \end{matrix} \quad \begin{matrix} \rightarrow \\ t-t_0 \\ (t-15) \end{matrix}$$

