
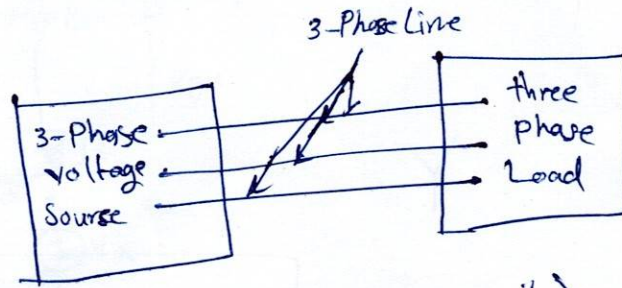


Three-Phase

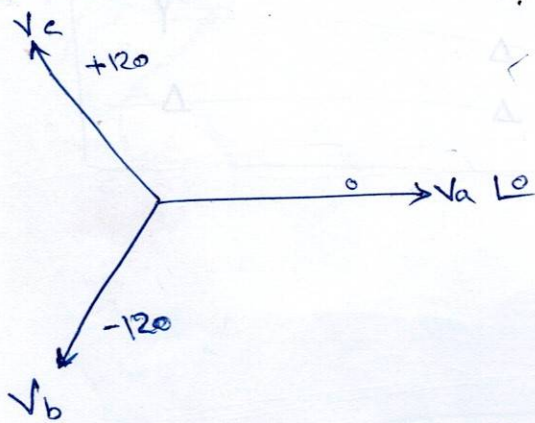

(a basic 3-Phase circuit)


Positive (abc) sequence



I.

$$\begin{aligned} V_a &= V_m \angle 0^\circ \\ V_b &= V_m \angle -120^\circ \\ V_c &= V_m \angle +120^\circ \end{aligned}$$

Negative (acb) sequence

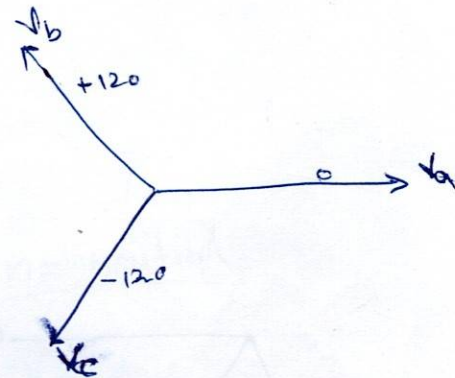

$$\begin{aligned} V_a &= V_m \angle 0^\circ \\ V_b &= V_m \angle +120^\circ \\ V_c &= V_m \angle -120^\circ \end{aligned}$$

Source → Line → Load

$$V_a + V_b + V_c = 0$$

* مواصفات 3-phase

* توليد الطاقة ونقلها وتوزيعها بكميات كبيرة يتطلب ربطا بطريقة 3-Phase بدلا من single phase.
 * توليد power عالي جدا.
 * تعتبر على مصادر الفولتية.



* 3-طافات مرتبطة مع بعض. مصنوعة بطريقة identical متساوية من حيث المادة وعدد اللفات والاقطان.

* الفولتيات تكون متساوية من حيث القيمة والتردد ما عدا الطور (phase) بـ 120° .


* shift by 120°

طريقة الربط للقيمة Δ - Y - Δ

وكذلك بالنسبة للـ Load

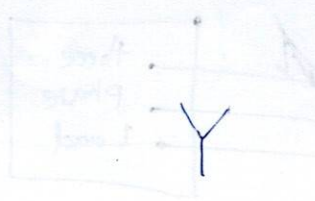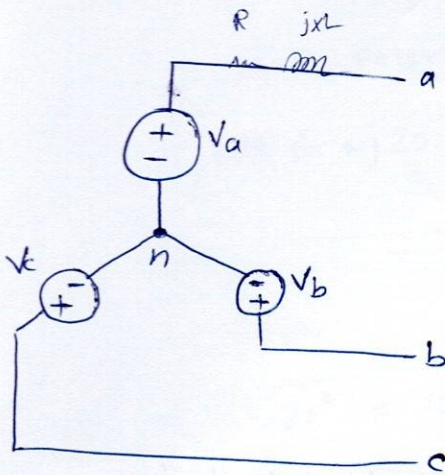


Source	Load
Y	Y
Y	Δ
Δ	Y
Δ	Δ

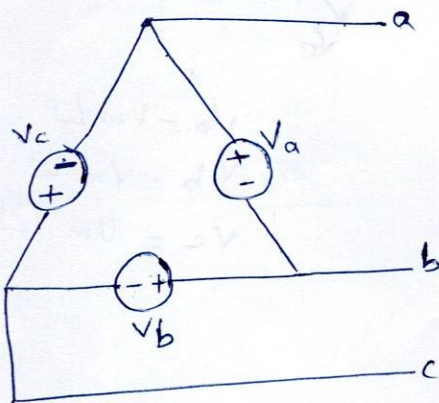


طريقة الربط للقيمة Δ - Y - Δ ونكمل الحل .

الف ممتد على impedance Z . يعنى مقاومة ومحاثة $Z_g = (R + jXL)$ مائدة داخلية

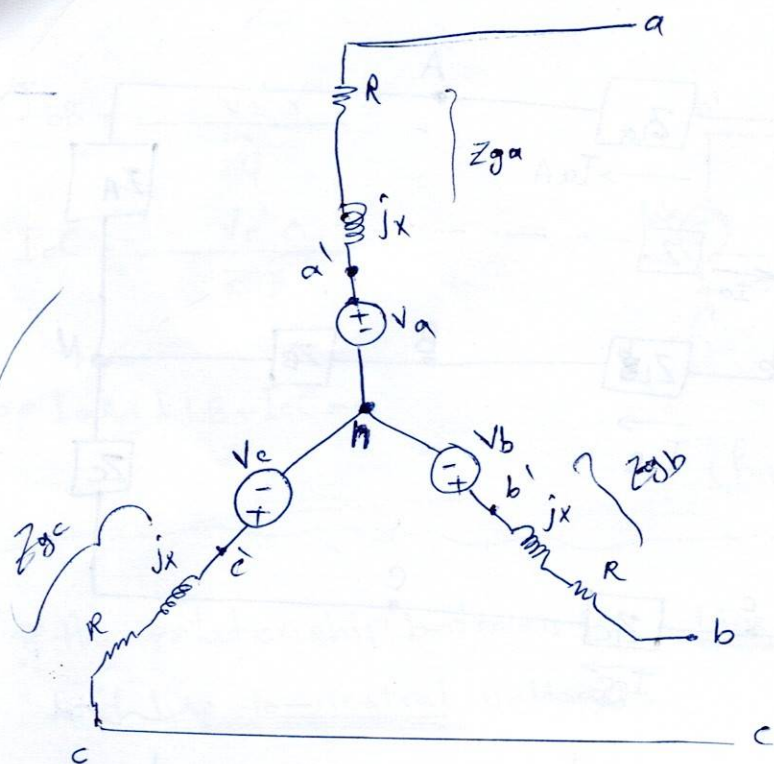
لا تعتبر المصاحبة خارج المصدر ، لتحليل الدائرة .



$n = \text{neutral}$

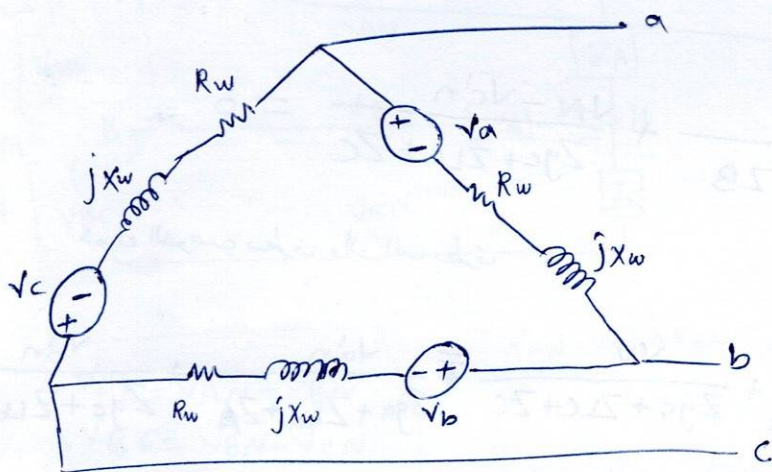

Analysis of the Wye-Wye circuit (Y-Y)

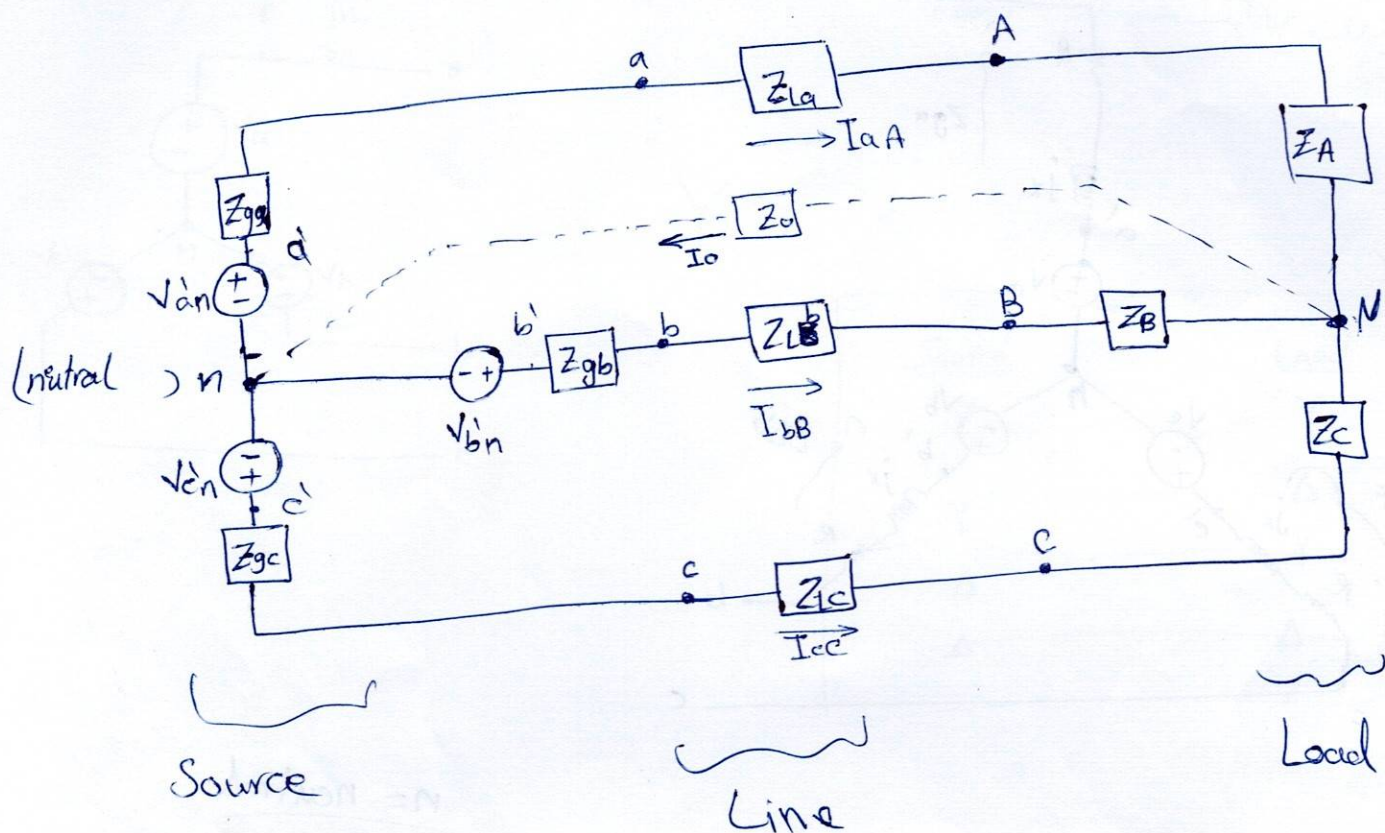

الاصرف الصغيرة للـ
الاصرف الكبيرة للـ

معادلة

$$\frac{V_N}{Z_0} + \frac{V_N - V_{an}}{Z_{ga} + Z_{La} + Z_A} + \frac{V_N - V_{bn}}{Z_{gb} + Z_{Lb} + Z_B} + \frac{V_N - V_{cn}}{Z_{gc} + Z_{Lc} + Z_C} = 0$$

قول الموصف بطر والـ الب طرف

$$\frac{V_N}{Z_0} + \frac{V_N}{Z_{ga} + Z_{La} + Z_A} + \frac{V_N}{Z_{gb} + Z_{Lb} + Z_B} + \frac{V_N}{Z_{gc} + Z_{Lc} + Z_C} = \frac{V_{an}}{Z_{ga} + Z_{La} + Z_A} + \frac{V_{bn}}{Z_{gb} + Z_{Lb} + Z_B} + \frac{V_{cn}}{Z_{gc} + Z_{Lc} + Z_C}$$

$$+ \frac{V_{cn}}{Z_{gc} + Z_{Lc} + Z_C}$$

$$Z_0 = Z_{ga} + Z_{La} + Z_A = Z_{gb} + Z_{Lb} + Z_B = Z_{gc} + Z_{Lc} + Z_C$$

$$V_N \left(\frac{1}{Z_0} + \frac{3}{Z_0} \right) = \frac{V_{an}}{Z_0} + \frac{V_{bn}}{Z_0} + \frac{V_{cn}}{Z_0}$$


$$= \frac{V_{an} + V_{bn} + V_{cn}}{Z_0}$$

(5)

$$I_{aA} = \frac{V_{a'n}}{Z_{\phi}}$$

$$I_{bB} = \frac{V_{b'n}}{Z_{\phi}}$$

$$I_{cC} = \frac{V_{c'n}}{Z_{\phi}}$$

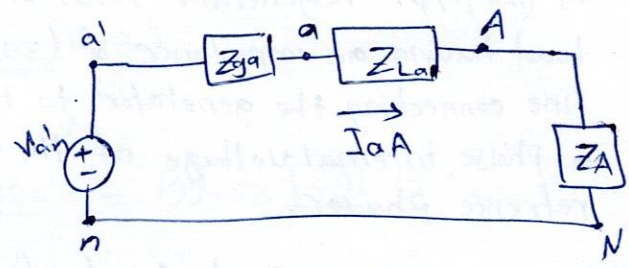



(single phase equivalent ckt.)

$$I_o = I_{aA} + I_{bB} + I_{cC} = 0$$

(First step in analyzing a 3-phase ckt.)

* the relationship between the Line-to-line voltages and line-to-neutral voltages.

لقد جزء load في كل دائرة Y.

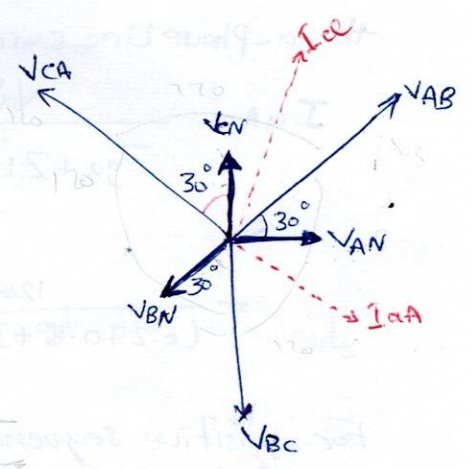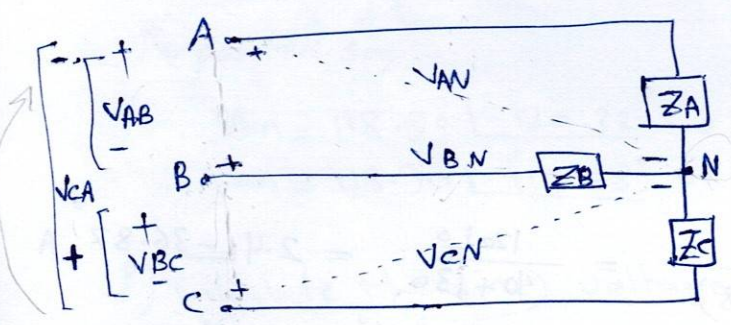

$$\begin{aligned} V_{AB} &= V_{AN} - V_{BN} \\ V_{BC} &= V_{BN} - V_{CN} \\ V_{CA} &= V_{CN} - V_{AN} \end{aligned}$$

$$\begin{aligned} V_{AN} &= V_{AB} + V_{BN} \\ V_{BN} &= V_{BC} + V_{CN} \\ V_{CN} &= V_{CA} + V_{AN} \end{aligned}$$

* V_{AB}, V_{BC}, V_{CA} —> Line-to-Line voltages

* V_{AN}, V_{BN}, V_{CN} —> Line-to-neutral voltages


$$V_{AB} = (\sqrt{3} \angle 30^\circ) V_{AN} \quad \text{positive sequence}$$

$$V_{BC} = V_{AB} \angle -120^\circ$$

$$V_{CA} = V_{AB} \angle +120^\circ$$

Example: A balanced 3-phase Y-connected generator with positive sequence has an impedance of $(0.2 + j0.5) \Omega/\phi$ and an internal voltage of $(120) V/\phi$. The generator feeds a balanced 3-phase Y-connected load having an impedance of $(39 + j28) \Omega/\phi$. The impedance of the line connecting the generator to the load is $(0.8 + j1.5) \Omega/\phi$. The a-phase internal voltage of the generator is specified as the reference phasor.

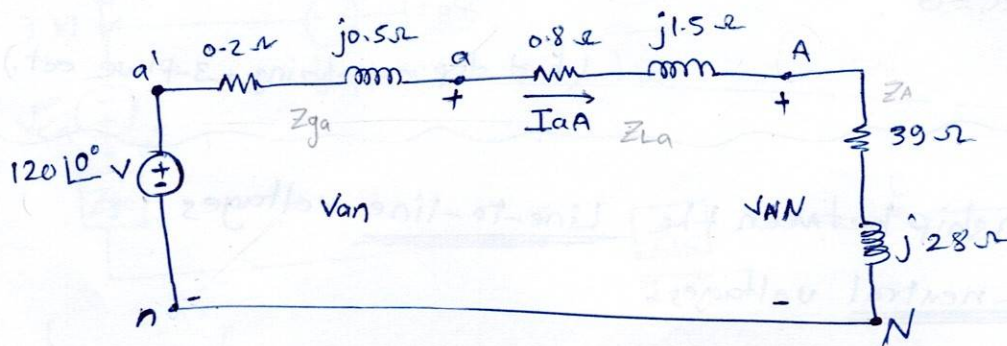a) construct the a-phase equivalent ckt. of the system.



b) Calculate the three Line current I_{aA}, I_{bB}, I_{cC} .

the a-phase Line current is

$$I_{aA} = \frac{V_{an}}{Z_{ga} + Z_{la} + Z_A}$$

$$= \frac{120 \angle 0^\circ}{(0.2 + 0.8 + 39) + j(0.5 + 1.5 + 28)} = \frac{120 \angle 0^\circ}{40 + j30} = 2.4 \angle -36.87^\circ \text{ A}$$

$50 \angle 36.86^\circ$

For a positive sequence phase $\rightarrow$

$$I_{bB} = 2.4 \angle -36.87^\circ - 120^\circ = 2.4 \angle -156.87^\circ \text{ A}$$

$$I_{cC} = 2.4 \angle -36.87^\circ + 120^\circ = 2.4 \angle 83.13^\circ \text{ A}$$

c) Calculate the three phase Voltage at load, V_{AN}, V_{BN}, V_{CN} .

$$V_{AN} = Z_A \times I_{aA} = (39 + j28) \times (2.4 \angle -36.87^\circ) = 115.22 \angle -1.19^\circ \text{ V}$$

$$V_{BN} = 115.22 \angle -1.19^\circ - 120^\circ = 115.22 \angle -121.19^\circ \text{ V}$$

$$V_{CN} = 115.22 \angle -1.19^\circ + 120^\circ = 115.22 \angle 118.81^\circ \text{ V}$$

calculate the line voltage V_{AB}, V_{BC}, V_{CA} at the terminals of the load.

$$\begin{aligned} \text{Line } V_{AB} &= (\sqrt{3} \angle 30^\circ) V_{AN} \text{ --- phase} \\ &= (\sqrt{3} \angle 30^\circ) * (115.22 \angle -1.19^\circ) \\ &= 199.58 \angle 28.81^\circ \text{ V.} \end{aligned}$$

$$V_{BC} = 199.58 \angle 28.81 - 120^\circ = 199.58 \angle -91.19^\circ \text{ V.}$$

$$V_{CA} = 199.58 \angle 28.81 + 120^\circ = 199.58 \angle 148.81^\circ \text{ V.}$$

e) calculate the phase voltages at the terminals of the generator V_{an}, V_{bn}, V_{cn} .

$$\begin{aligned} V_{an} &= V_a'n - V_{ga} \\ &= 120 \angle 0^\circ - [(0.2 + j0.5) * (2.4 \angle -36.87^\circ)] \\ &= 120 \angle 0^\circ - 1.29 \angle 31.33^\circ \\ &= 118.90 - j0.67 \\ &= 118.90 \angle -0.32^\circ \text{ V.} \end{aligned}$$

For positive seq.

$$\begin{aligned} V_{bn} &= 118.90 \angle -120.32^\circ \text{ V.} \\ V_{cn} &= 118.90 \angle 119.68^\circ \text{ V.} \end{aligned}$$

f) Calculate the line voltages V_{ab}, V_{bc}, V_{ca} at the terminals of the generator.

$$\begin{aligned} V_{ab} &= (\sqrt{3} \angle 30^\circ) V_{an} \\ &= (\sqrt{3} \angle 30^\circ) (118.90 \angle -0.32^\circ) \\ &= 205.94 \angle 29.68^\circ \text{ V.} \end{aligned}$$

$$V_{bc} = 205.94 \angle -90.32^\circ \text{ V.}$$

$$V_{ca} = 205.94 \angle 149.68^\circ \text{ V.}$$

g) Repeat (a — f) for a negative sequence phase.

~~h)~~


* Analysis of the Wye-Delta ckt. Y-Δ

$$Z_Y = \frac{Z_\Delta}{3}$$

$$I_{AB} = \left(\frac{1}{\sqrt{3}} \angle 30^\circ \right) I_{aA}$$

$$I_{AB} = I_\phi$$


positive

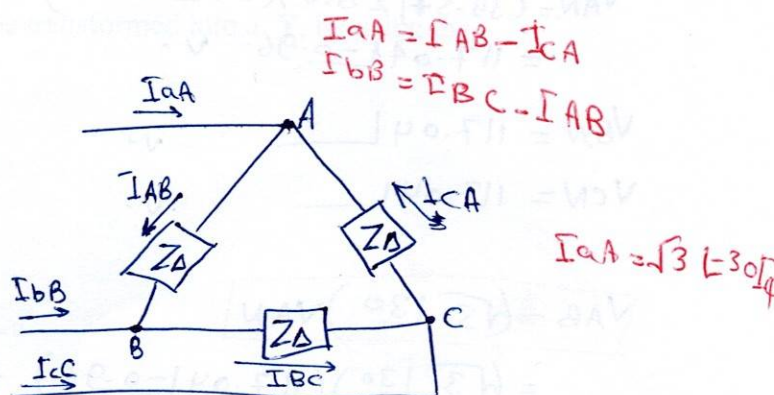

Ex: The Y-connected Source in Ex 1 feeds a Δ-connected load through a distribution line having an impedance of $(0.3 + j0.9) \Omega/\phi$. The load impedance is $(118.5 + j85.8) \Omega/\phi$. Use the a-phase internal voltage of the generator as the reference.

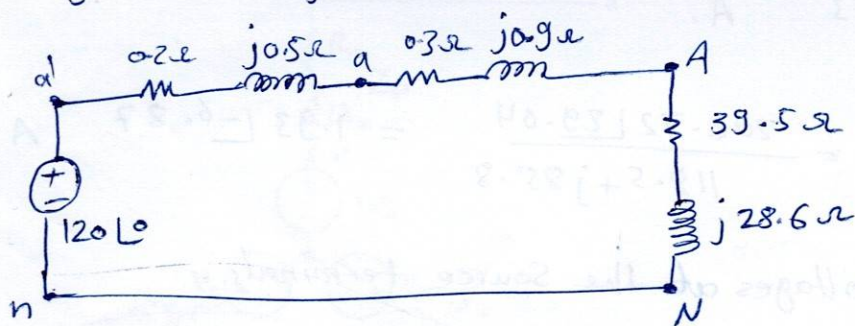a) Construct a single-phase equivalent circuit of the 3-phase system.

$$Z_Y = \frac{Z_\Delta}{3} = \frac{118.5 + j85.8}{3} = 39.5 + j28.6 \Omega/\phi$$



b) calculate the line current I_{aA} , I_{bB} , I_{cC} .

$$I_{aA} = \frac{V_{an}}{Z_{ga} + Z_{La} + Z_A}$$

$$= \frac{120 \angle 0^\circ}{(0.2 + 0.3 + 39.5) + j(0.5 + 0.9 + 28.6)}$$

$$= \frac{120 \angle 0^\circ}{40 + j30} = 2.4 \angle -36.87^\circ \text{ A}$$

$$I_{bB} = 2.4 \angle -156.87^\circ \text{ A}, \quad I_{cC} = 2.4 \angle 83.13^\circ \text{ A}$$

c) calculate the phase voltages at the load terminals.

$$V_{AN} = (39.5 + j28.6)(24 \angle -36.87^\circ) \\ = 117.04 \angle -0.96^\circ \text{ V.}$$

$$V_{BN} = 117.04 \angle \text{---}^\circ \text{ V.}$$

$$V_{CN} = 117.04 \angle \text{---}^\circ \text{ V.}$$

$$V_{AB} = (\sqrt{3} \angle 30^\circ) V_{AN}$$

$$= (\sqrt{3} \angle 30^\circ)(117.04 \angle -0.96^\circ) = 202.72 \angle 29.04^\circ \text{ V.}$$

$$V_{BC} = 202.72 \angle -90.96^\circ \text{ V.}$$

$$V_{CA} = 202.72 \angle 149.04^\circ \text{ V.}$$

d) Calculate the Phase current of the load.

$$Y \rightarrow I_\phi = I_L$$

$$\Delta \rightarrow V_\phi = V_L$$

$$I_{AB} = \left(\frac{1}{\sqrt{3}} \angle 30^\circ \right) I_{aA} = 1.39 \angle -6.87^\circ \text{ A}$$

$$I_{BC} = 1.39 \angle -126.87^\circ \text{ A}$$

$$I_{CA} = 1.39 \angle 113.13^\circ \text{ A.}$$

$$\text{or} \rightarrow I_{AB} = \frac{V_{AB}}{Z_\phi} = \frac{202.72 \angle 29.04^\circ}{118.5 + j85.8} = 1.93 \angle -6.87^\circ \text{ A}$$

e) Calculate the line voltages at the source terminals.


$$V_{an} = (39.8 + j29.5)(2.4 \angle -36.87^\circ) = I_{aA}(Z_{La} + Z_A) \\ = 118.90 \angle -0.32^\circ \text{ V.}$$

The line voltage V_{ab} is

$$V_{ab} = (\sqrt{3} \angle 30^\circ) V_{an} \\ = 205.94 \angle 29.68^\circ \text{ V.}$$

$$V_{bc} = 205.94 \angle -90.32^\circ \text{ V.}$$
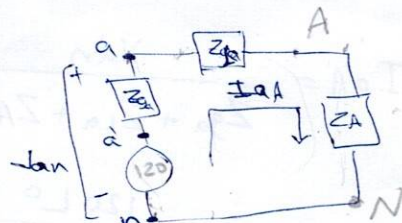
$$V_{ca} = 205.94 \angle 149.68^\circ \text{ V.}$$



طريقة اخرى (لدي)

$$V_{an} = V_{an} - V_{ga} \\ V_{ga} = I_{aA} \times Z_{ga} \\ = (2.4 \angle -36.87^\circ)(0.2 + j0.5) \\ = 1.29 \angle -35.68^\circ \\ V_{an} = 120 \angle 0^\circ - 1.29 \angle -35.68^\circ \\ = 120 - 1.047 - j0.75 \\ = 118.95 \angle -0.75^\circ \\ = 118.95 \angle -0.36^\circ \text{ V.}$$